

CCD CAMERA COOKBOOK

Table of Contents

1. Introduction to CCD Cameras

- 1.1. What You Are Building
- 1.2. What You Will Need
- 1.3. How to Find Parts
- 1.4. Prepare a Work Area
- 1.5. Work Safely!

2. What a CCD Camera Does

- 2.1. What a CCD Camera Is
- 2.2. What Each Part of the Camera Does
- 2.3. What CCD Images Look Like
- 2.4. How You Will Use Your CCD Camera

3. How the CCD Camera Works

- 3.1. How a CCD Chip Works
 - 3.1.1. CCD Chip Operation Theory
 - 3.1.1.1. The Organization of the TC211
 - 3.1.1.2. The TC245 CCD Chip
 - 3.1.2. CCD Charge Detection Amplifiers
 - 3.1.2.1. Charge Detection in the TC211
 - 3.1.2.2. Charge Detection in the TC245
 - 3.1.3. Acquiring an Image from the CCD Chip
 - 3.1.3.1. Normal Image Acquisition
 - 3.1.3.2. Internal Binning
 - 3.1.3.3. External Binning
 - 3.1.3.4. Combination Binning
 - 3.1.3.5. Double Sampling
 - 3.1.3.6. Pseudo-Shuttering
- 3.2. How the Support Electronics Work
 - 3.2.1. Passing Timing Signals to the CCD
 - 3.2.2. Supplying Voltages for the CCD
 - 3.2.3. Inverting and Digitizing the Image
 - 3.2.4. Returning the Image to the Computer
- 3.3. How Software Controls the Camera
 - 3.3.1. Controlling the Cookbook 211
 - 3.3.2. Controlling the Cookbook 245
- 3.4. How the Cooling System Works
 - 3.4.1. Methods of Cooling
 - 3.4.2. How the Peltier Module Works
 - 3.4.3. How the Cooling System Works

4. Starting Your CCD Camera

- 4.1. Order Electronic Components First
- 4.2. The Best Order for Building Parts
- 4.3. How Long Will It Take to Build?
- 4.4. How Much Will It Cost?

5. Building the Power Supply

- 5.1. What the Power Supply Does
- 5.2. How the Power Supply Works
- 5.3. How to Build the Power Supply
 - 5.3.1. Construct the Wooden Case
 - 5.3.2. Place the Large Components

- 5.3.3. Wiring the AC Components
 - 5.3.3.1. AC Wiring Rules
 - 5.3.3.2. AC Wiring for the Power Supply
- 5.3.4. Wiring the DC Components
 - 5.3.4.1. Wiring the $\pm 15\text{VDC}$ and Pump Supplies
 - 5.3.4.2. Test the $\pm 15\text{VDC}$ and Pump Supplies
 - 5.3.4.3. Complete the Peltier Supply
 - 5.3.4.4. Test the Peltier Supply

6. Building the Camera Interface

- 6.1. What the Interface Card Does
- 6.2. How the Interface Works
 - 6.2.1. How Control Signals Reach the Camera
 - 6.2.2. How the Voltage Regulators Work
 - 6.2.3. Digitizing Signals from the Camera
 - 6.2.4. How the Interface Returns Images
- 6.3. Constructing the Interface Card
 - 6.3.1. The Printer Port Ribbon Cable
 - 6.3.2. The $\pm 15\text{VDC}$ Power Cable
 - 6.3.3. Prepare the Interface Card Box
 - 6.3.4. Building the Interface with CARD.EXE
 - 6.3.5. CARD.EXE Test Sequences
 - 6.3.6. Install the Interface Card in Its Box
- 6.4. Constructing the Preamplifier Card
 - 6.4.1. What the Preamplifier Does
 - 6.4.2. How the Clock Drivers Work
 - 6.4.3. How the Preamplifier Works
- 6.5. Assembling the Preamplifier Card
 - 6.5.1. Construct Connectors and Cables
 - 6.5.2. PREAMP.EXE Test Sequences
 - 6.5.3. Fabricate the Preamp Cover
- 6.6. Package the Interface Card
- 6.7. What Comes Next?

7. Building the Camera Head

- 7.1. What the Camera Head Does
- 7.2. How the Camera Head Works
- 7.3. Constructing the Camera Head
 - 7.3.1. Machine the Camera Head
 - 7.3.1.1. Turn the Cap and Heat Exchanger
 - 7.3.1.2. Machine the Eyepiece Tube
 - 7.3.1.3. Turn the Camera Housing
 - 7.3.1.4. Drill and Mill the Camera Housing
 - 7.3.1.5. Mark the Heat Exchanger Drill Holes
 - 7.3.1.6. Drill and Mill the Heat Exchanger
 - 7.3.1.7. Cookbook 211 Cold Finger
 - 7.3.1.8. Cookbook 245 Cold Finger
 - 7.3.1.9. Turn the End Plate
 - 7.3.1.10. Make Two Cover Brackets
 - 7.3.2. Planarize Mating Surfaces
- 7.4. Integrating the Components
 - 7.4.1. Camera Body Assembly
 - 7.4.2. Install the J2/J3 Electrical Sockets
 - 7.4.3. Bond a Socket to the Cold Finger
 - 7.4.4. Mount the Optical Window
 - 7.4.5. Assemble the Heat Exchanger
 - 7.4.6. Install the Peltier Cooler

- 7.5. Final Assembly of the Camera Body
 - 7.5.1. Install the TC211 CCD
 - 7.5.2. Socket-Test the TC211 CCD
 - 7.5.3. Install the TC245 CCD
 - 7.5.2. Testing the TC245 CCD
- 7.6. First Light!
- 7.7. Clean and Close the Camera Body
- 7.8. Install the Preamplifier Cover
- 7.9. What You Have Done and What Remains

8. Building the Coolant System

- 8.1. What Cooling a CCD Does
- 8.2. How the Liquid Coolant System Works
- 8.3. Building the Coolant System
 - 8.3.1. Form the Copper Coil
 - 8.3.2. Assemble the Cable Harness
 - 8.3.3. Mount the Pump and Coil
- 8.4. Test the Liquid Coolant System

9. Using the Camera Software

- 9.1. What the Software Does
- 9.2. How the Software Works
 - 9.2.1. Starting AP211 and AP245
 - 9.2.2. Image and Data Files
 - 9.2.2.1. Image Formats for the Cookbook
 - 9.2.2.2. Image Formats for the Cookbook
- 9.3. The AP211 and AP245 Functions
 - 9.3.1. The Main Menu
 - 9.3.2. The Integrate-Image Command
 - 9.3.3. The Multiple-Images Command
 - 9.3.4. The Display-Image Command
 - 9.3.5. The Focus/Find Command 122
 - 9.3.6. The Copy-as-Dark-Frame Command
 - 9.3.7. The Autoguide Command
 - 9.3.8. The Options Command
 - 9.3.9. The Set-File-Path Command
 - 9.3.10. The Store-Image Command
 - 9.3.11. The Get-Image Command
 - 9.3.12. The Export-to-FITS Command
 - 9.3.13. The Quit Command
- 9.4. Practice Makes Perfect

10. Integrating and Testing

- 10.1. Putting the System Together
- 10.2. Critical Camera Check-Out
 - 10.2.1. Test Step 1: Ready Yourself!
 - 10.2.2. Test Step 2: Set the Ref Level
 - 10.2.3. Test Step 3: Set Delay Timing
 - 10.2.4. Test Step 4: Check Cooling
 - 10.2.5. Test Step 5: Check for RF Noise
 - 10.2.6. Test Step 6: Camera Burn-In
- 10.3. Shoot Your First CCD Image

11. Enjoying Your CCD Camera

- 11.1. How to Use a CCD for Imaging
 - 11.1.1. Finding
 - 11.1.2. Focusing

- 11.1.3. Following
- 11.2. Making Astronomical Images
 - 11.2.1. Choosing the Integration Time
 - 11.2.2. Making Dark Frames
 - 11.2.3. Flat-Field Frames
 - 11.2.4. Making Multiple Images
- 11.3. Image Processing
 - 11.3.1. Image Calibration
 - 11.3.2. Image Analysis
 - 11.3.3. Scaling Image Data
 - 11.3.4. Filtering and Image Restoration
- 11.4. Basic CCD Troubleshooting
 - 11.4.1. What Can Go Wrong?
 - 11.4.2. Regular Maintenance
 - 11.4.3. If Your CCD Fails...

12. CCDs in Amateur Astronomy

- 12.1. The CCD: A Cheap Linear Detector
- 12.2. The CCD for Making Pretty Pictures
- 12.3. The CCD for Obtaining “Real Data”

Appendix A: Personal and ESD Safety

- A.1. Danger! House Current
- A.2. Electrostatic Discharge
- A.3. Always Check for Correct Wiring
- A.4. Never Forget Safety!

Appendix B: Building Electronic Circuits

- B.1. Identifying Electronic Components
- B.2. A Lesson on Soldering
- B.3. Get a Good Meter
- B.4. Troubleshooting with a Multimeter
 - B.4.1. Measuring Diodes
 - B.4.2. Measuring Transistors
 - B.4.3. Measuring Capacitors
 - B.4.4. Measuring Resistors
 - B.4.5. Measuring Integrated Circuits
 - B.4.6. Measuring Regulators
 - B.4.7. Substituting Parts

Appendix C: Improving Your CCD Camera

- C.1. Add One-Plug Convenience
- C.2. Extend Your Cables
- C.3. Improve Noise Immunity
- C.4. Optimize Charge Transfer
- C.5. Beef Up the Cooling System
- C.6. Run on Battery Power
- C.7. Use a Commercial Power Supply
- C.8. Open-Collector Parallel Ports

Appendix D: Converting the 211 to a 245

- D.1. Changes to the Interface Card
- D.2. Changes to the Preamplifier Card
- D.3. Install the TC245

Appendix E: Constructing an Autoguider

- E.1. Building the Serial Port Interface

E.2. Operating the Autoguider

References and Resources

Technical Notes on the CCD Images

Index